

## 《数字逻辑》实验报告


姓名		年级	2022 级
学号		专业、班级	计算机科学与技术 (卓越) 1 班
实验名称	实验十三 流水线加法器		
实验时间	2023. 11. 9	实验地点	计算机机房 DS1410
实验成绩		实验性质	<input type="checkbox"/> 验证性 <input checked="" type="checkbox"/> 设计性 <input type="checkbox"/> 综合性
<p>教师评价：</p> <p><input type="checkbox"/>算法/实验过程正确；   <input type="checkbox"/>源程序/实验内容提交   <input type="checkbox"/>程序结构/实验步骤合理；</p> <p><input type="checkbox"/>实验结果正确；   <input type="checkbox"/>语法、语义正确；   <input type="checkbox"/>报告规范；</p> <p>评语：</p> <p>评价教师签名（电子签名）：</p>			
<p>一、实验目的</p> <p>1、掌握寄存器的设计与应用。</p> <p>2、学习和掌握流水线加法器的设计与实现。</p>			

## 二、实验项目内容

- 1、设计并实现一个 32 位 2 级流水线加法器，并下板验证。
- 2、主要从 RTL 电路分析、仿真波形、开发板资源使用情况等方面与实验六中的加法器和系统自带“+”加法器进行比较。
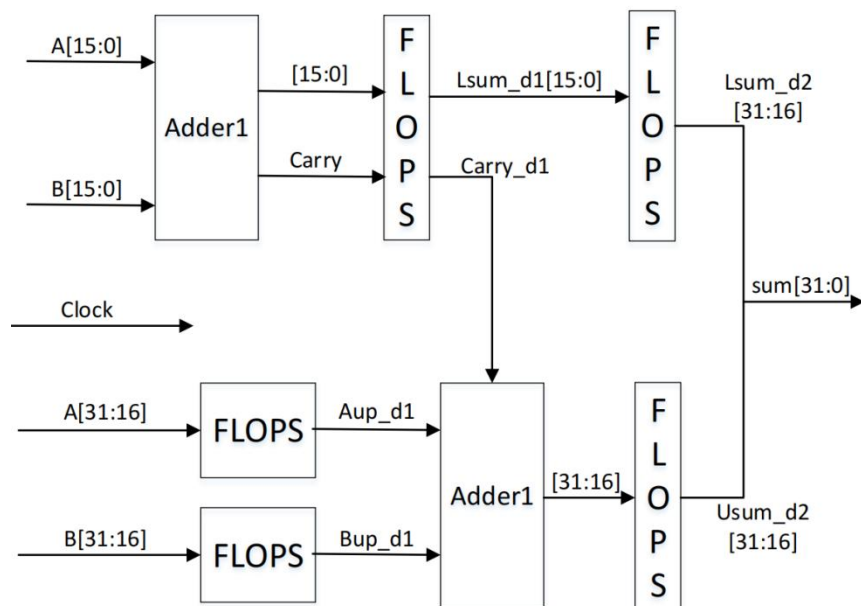
## 三、实验设计（实验原理、真值表、原理图等）

32 位的 2 级流水线加法器使用两个 16 位加法器，其中第一个加法器执行低 16 位的加法，而第二个加法器执行高 32 位的加法，电路结构图如下图所示（供参考）。



具体的实验原理为，两个 16 位加减法器同时进行加减法，从而使原本串行的实验并行完成，提高了加减法的效率

## 四、实验过程或算法（关键步骤、核心代码注解等）

### （1）代码模块详解

①顶层模块（调用三十二位加减法器，控制数码管的显示）

```
module topuse(  
    input clk,  
    input reset,
```

```

input [3:0] hex0, //第一个数码管显示的数字
input [3:0] hex1,
output reg [3:0] an, //片选,使能端
output reg [7:0] sseg, //段选, 最后数码管的输出
input c0,
output C32,
    output Gm,
    //进位产生标志 (该输出为 1 时, 不管 c0 真值情况, 一定会进位)
    output Pm
    //进位传递标志 (该输出为 1 时, 需要 c0 为 1, 才会进位)
);

    wire [32:1] hex3;

    parameter N = 18; //使用低 16 位对 50Mhz 时钟进行分频(50MHZ/2^16)
    reg [N-1:0] regN; //高两位作为控制信号, 低 16 位为计数器, 对时钟进
行分频
    reg [3:0] hex_in; //段选控制信号
    reg dp;
    wire dp_operator, dp_result;

    j32j a(
        .in1({28'b0,hex0}),
        .in2({28'b0,hex1}),
        .add_sub(c0),
        .Gm(Gm),
        .Pm(Pm),
        .sum(hex3),
        .c32(C32),
        .clk(clk),
        .rst_n(reset)
    );

    assign dp_operator=c0,
        dp_result=c0&&(~C32);

```

`always@(posedge clk, posedge reset)`//低十六位开始计数，当计数到前两位时显示数码管

```
begin
    if(reset)
        regN <= 0;
    else
        regN <= regN + 1;
end
```

`always@ (*)`

```
begin
    case(regN[N-1:N-2])
        2'b00:begin
            an = 4'b0111; //选中第 1 个数码管
            hex_in = hex0; //数码管显示 hex0 输入的数字;
            dp = 0; //控制该数码管的小数点的亮灭
        end
        2'b01:begin
            an = 4'b1011; //选中第二个数码管
            hex_in = hex1; //数码管显示 hex1 输入的数字;
            dp = dp_operator;
        end
        2'b10:begin
            an = 4'b1110; //选中第三个数码管
            hex_in = hex3[4:1]; //数码管显示 hex3 输入的数字;
            dp = dp_result;
        end
        default:
            begin
                an = 4'b1110; //选中第四个数码管
                hex_in = hex3[4:1]; //数码管显示的数字由 hex_in 控制，显示
                dp = dp_result;
            end
    endcase
end
```

```

end

endcase

end

always@(*)
begin
    case(hex_in)//数码管的显示
        4'h0: sseg[6:0] = 7'b0000001; //共阳极数码管
        4'h1: sseg[6:0] = 7'b1001111;
        4'h2: sseg[6:0] = 7'b0010010;
        4'h3: sseg[6:0] = 7'b0000110;
        4'h4: sseg[6:0] = 7'b1001100;
        4'h5: sseg[6:0] = 7'b0100100;
        4'h6: sseg[6:0] = 7'b0100000;
        4'h7: sseg[6:0] = 7'b0001111;
        4'h8: sseg[6:0] = 7'b0000000;
        4'h9: sseg[6:0] = 7'b0001100;
        4'ha: sseg[6:0] = 7'b0001000;
        4'hb: sseg[6:0] = 7'b1100000;
        4'hc: sseg[6:0] = 7'b1110010;
        4'hd: sseg[6:0] = 7'b1000010;
        4'he: sseg[6:0] = 7'b0110000;
        4'hf: sseg[6:0] = 7'b0111000;
        default: sseg[6:0] = 7'b0111000;

    endcase

    sseg[7] = ~dp;

end

```

endmodule

②32 位加减法器模块（调用三十二位加法器模块，完成减法时的输出）

```

module j32j(
    input [32:1]in1,
    input [32:1]in2,

```

```

        input add_sub,
        output Gm,
        output Pm,
        output [32:1]sum,
        output c32,
        input  clk,
        input  rst_n
    );
    wire [32:1] in1_exp;
    wire [32:1] in2_exp;
    wire cin;
    wire [32:1]sum_temp1;
    wire [32:1]sum_temp2;

    assign in1_exp = {in1};
    assign in2_exp = add_sub? ~{in2}: {in2};    //做减法时，需要对 in2 进行补码运算
    assign cin = add_sub;                      //对 in2 进行 2 的补码运算

    // 因为对输入进行了扩位,所以 WIDTH 需要加 1，在输出的时候会被截位，但对结果无影响
    adder32 adder32(//调用 32 位加法器进行运算
        .A( in1_exp ),
        .B( in2_exp ),
        .c0( cin ),
        .Gm(Gm),
        .Pm(Pm),
        .S( sum_temp1 ),
        .C32(c32),
        .clk(clk),
        .rst_n(rst_n)
    );

    adder32_clu a(//调用加法器取补码
        .A( ~sum_temp1 ),

```

```

.B( 0 ),
.c0( 1'b1 ),
.Gm(),
.Pm(),
.S( sum_temp2 ),
.C32()
);

```

`assign sum = (add_sub&(~c32)) ? {sum_temp2} : {sum_temp1};` //做减法时，若结果为负数，需要对 in2 进行补码运算

Endmodule

③32 位加法器模块（32 位加法器模块调用 32 位流水线加法器模块，32 位流水线加法器由两个并行的 16 位 CLA(carry lookahead unit)实现）

```

module adder32(A,B,c0,Gm,Pm,S,C32,clk,rst_n);

```

```

    input [32:1] A;
        input [32:1] B;
        input c0;
        output Gm;
        output Pm;
        output [32:1] S;
        output C32;
        input  clk;
        input  rst_n;

        wire px1,gx1,px2,gx2;
        wire c16;

```

```

        adder_pipeline_32bit_2level adder32_to_pipeline_32bit(//调用 32 位流水线
加法器
        .FinalSum(S),
        .co(C32),
        .A(A),

```

```

        .B(B),
        .ci(c0),
        .clk(clk),
        .reset(rst_n),

        .px1(px1),
        .gx1(gx1),
        .px2(px2),
        .gx2(gx2)
    );

```

**assign**//完成进位等的计算

```
Gm = gx2 ^ (gx1 & px2) ^ (px1 & c0),
```

```
Pm = px1 & px2;
```

**endmodule**

//adder\_pipeline\_32bit\_2level 32 位流水线模块代码

```
module adder_pipeline_32bit_2level(A,B,clk,reset,FinalSum,ci,co,px1,gx1,px2,gx2);
```

```
input clk,reset;
```

```
input [31:0] A,B;
```

```
output [31:0] FinalSum;
```

```
input      ci;
```

```
output     co;
```

```
output wire px1,gx1,px2,gx2;
```

```
wire carry_d1;
```

```
reg [15:0] Lsum_d1;
```

```
wire [15:0] Lsum_d1_nxt;
```

```
reg [15:0] Lsum_d2;
```

```
reg [15:0] Aup_d1,Bup_d2;
```

```
reg [15:0] Usum_d2;
```

```
wire [15:0] Usum_d2_nxt;
```

```
wire [31:0] FinalSum;
```



```
wire c16;  
assign c16 = gx1 ^ (px1 && ci),  
        co = gx2 ^ (px2 && c16);
```

```
CLA_16 CLA1(          //后十五位加法  
    .A(A[15:0]),  
    .B(B[15:0]),  
    .c0(ci),  
    .S(Lsum_d1_nxt),  
    .px(px1),  
    .gx(gx1)  
);
```

```
CLA_16 CLA2(          //前 15 位加法，赋值在后面的 always 块中  
    .A(Aup_d1),  
    .B(Bup_d2),  
    .c0(carry_d1),  
    .S(Usum_d2_nxt),  
    .px(px2),  
    .gx(gx2)  
);
```

```
assign carry_d1 = c16;  
assign FinalSum = {Usum_d2,Lsum_d2};
```

```
always@(posedge clk or negedge reset)begin//对中间变量进行前 15 位的赋值  
    if(reset)begin  
        Lsum_d1 <= 0;
```

```

Lsum_d2 <= 0;
Aup_d1 <= 0;
Bup_d2 <= 0;
Usum_d2 <= 0;

end

else begin
    Lsum_d1 <= Lsum_d1_nxt;
    Lsum_d2 <= Lsum_d1[15:0];
    Aup_d1 <= A[31:16];
    Bup_d2 <= B[31:16];
    Usum_d2 <= Usum_d2_nxt;
end

end

Endmodule

```

#### ④16 位 CLA 模块（并行调用 4 个 4 位加法器）

```

module CLA_16(A,B,c0,S,px,gx);
    input [16:1] A;
        input [16:1] B;
        input c0;
        output gx,px;
        output [16:1] S;

        wire c4,c8,c12;
        wire Pm1,Gm1,Pm2,Gm2,Pm3,Gm3,Pm4,Gm4;

        adder_4 adder1( //1~4 位加法
            .x(A[4:1]),
            .y(B[4:1]),
            .c0(c0),
            .c4(),
            .F(S[4:1]),
            .Gm(Gm1),
            .Pm(Pm1)
        );

```

```
adder_4 adder2( //5~8 位加法
```

```
.x(A[8:5]),  
.y(B[8:5]),  
.c0(c4),  
.c4(),  
.F(S[8:5]),  
.Gm(Gm2),  
.Pm(Pm2)
```

```
);
```

```
adder_4 adder3( //9~12 位加法
```

```
.x(A[12:9]),  
.y(B[12:9]),  
.c0(c8),  
.c4(),  
.F(S[12:9]),  
.Gm(Gm3),  
.Pm(Pm3)
```

```
);
```

```
adder_4 adder4( //13~16 位加法
```

```
.x(A[16:13]),  
.y(B[16:13]),  
.c0(c12),  
.c4(),  
.F(S[16:13]),  
.Gm(Gm4),  
.Pm(Pm4)
```

```
);
```

```
//进位的计算
```

```
assign c4 = Gm1 ^ (Pm1 & c0),
```

```
c8 = Gm2 ^ (Pm2 & Gm1) ^ (Pm2 & Pm1 & c0),
```

```
c12 = Gm3 ^ (Pm3 & Gm2) ^ (Pm3 & Pm2 & Gm1) ^ (Pm3 & Pm2 &  
Pm1 & c0);
```

```

assign px = Pm1 & Pm2 & Pm3 & Pm4,
gx = Gm4 ^ (Pm4 & Gm3) ^ (Pm4 & Pm3 & Gm2) ^ (Pm4 & Pm3 & Pm2 & Gm1);

```

```

endmodule

```

④4 位加法器模块（并列调用 4 个 1 位加法器和 4 位 CLA 实现）

```

module adder_4(x,y,c0,c4,F,Gm,Pm);
    input [4:1] x;
        input [4:1] y;
        input c0;
        output c4,Gm,Pm;
        output [4:1] F;

        wire p1,p2,p3,p4,g1,g2,g3,g4;
        wire c1,c2,c3;
//各个位数同时相加，用四个 1 位加法器
        adder adder1(.X(x[1]),.Y(y[1]),.Cin(c0),.F(F[1]),.Cout());

        adder adder2(.X(x[2]),.Y(y[2]),.Cin(c1),.F(F[2]),.Cout());

        adder adder3(.X(x[3]),.Y(y[3]),.Cin(c2),.F(F[3]),.Cout());

        adder adder4(.X(x[4]),.Y(y[4]),.Cin(c3),.F(F[4]),.Cout());

        CLA CLA(.c0(c0),.c1(c1),.c2(c2),.c3(c3),.c4(c4),
                .p1(p1),.p2(p2),.p3(p3),.p4(p4),
                .g1(g1),.g2(g2),.g3(g3),.g4(g4)
                );

assign p1 = x[1] ^ y[1],p2 = x[2] ^ y[2],
p3 = x[3] ^ y[3],p4 = x[4] ^ y[4];

```

```
assign g1 = x[1] & y[1], g2 = x[2] & y[2],  
      g3 = x[3] & y[3], g4 = x[4] & y[4];
```

```
assign Pm = p1 & p2 & p3 & p4,  
      Gm = g4 ^ (p4 & g3) ^ (p4 & p3 & g2) ^ (p4 & p3 & p2 & g1);
```

```
endmodule
```

## ⑤1 位加法器模块和 4 位 CLA 模块

**module adder**(X,Y,Cin,F,Cout);//通过真值表列出输出进位与输入的逻辑公式即可实现 1 位加法器

```
input X,Y,Cin;
```

```
output F,Cout;
```

```
assign F = X ^ Y ^ Cin;
```

```
assign Cout = (X ^ Y) & Cin | X & Y;
```

```
endmodule
```

**module CLA**(c0,c1,c2,c3,c4,p1,p2,p3,p4,g1,g2,g3,g4);

//通过列真值表列出进位 c1,c2,c3,c4 的计算

```
input c0,g1,g2,g3,g4,p1,p2,p3,p4;
```

```
output c1,c2,c3,c4;
```

```
assign c1 = g1 ^ (p1 & c0),
```

```
      c2 = g2 ^ (p2 & g1) ^ (p2 & p1 & c0),
```

```
      c3 = g3 ^ (p3 & g2) ^ (p3 & p2 & g1) ^ (p3 & p2 & p1 & c0),
```

```
      c4=g4^(p4&g3)^(p4&p3&g2)^(p4&p3&p2&g1)^(p4&p3&p2&p1&c0);
```

```
endmodule
```

## (2) 仿真波形生成与观察

①仿真代码（由于顶层模块主要用于数码管的显示，仿真时实例化的模块是 j32-32 位加减法器模块，设置了不同的值用于

仿真)

```
module sim;
```

```
    reg [32:1] A;
```

```
    reg [32:1] B;
```

```
    reg c0;
```

```
    wire Gm;
```

```
    wire Pm;
```

```
    wire [32:1] S;
```

```
    wire c32;
```

```
    reg  clk;
```

```
    reg  rst_n;
```

```
    j32j d1( .in1(A),.in2(B),.add_sub(c0), .Gm(Gm),.Pm(Pm),  
            .sum(S),.c32(c32), .clk(clk),.rst_n(rst_n);
```

```
    initial begin
```

```
        clk  = 0;
```

```
        rst_n = 1;
```

```
        @(posedge clk) rst_n = 0;
```

```
        c0=0 ; A = 32'd1; B = 32'd1;
```

```
        @(posedge clk) c0=0 ; A = 32'd25; B = 32'd78;
```

```
        @(posedge clk) c0=0 ; A = 32'd3432523; B = 32'd3245325;
```

```
        @(posedge clk) c0=0 ; A = 32'd11111; B = 32'd11111;
```

```
        @(posedge clk) c0=0 ; A = 32'd9999; B = 32'd9999;
```

```
        @(posedge clk) c0=0 ; A = 32'd456; B = 32'd234;
```

```
        @(posedge clk); c0=0 ; A = 32'd245; B = 32'd678;
```

```
        @(posedge clk) c0=0 ; A = 32'd0; B = 32'd0;
```

```
        @(posedge clk); c0=0 ; A = 32'd25; B = 32'd78;
```

```
        @(posedge clk) c0=0 ; A = 32'd3423; B = 32'd3245325;
```

```
        @(posedge clk); c0=0 ; A = 32'd11111; B = 32'd11111;
```

```
        @(posedge clk) c0=0 ; A = 32'd99; B = 32'd9999;
```

```
        @(posedge clk) c0=0 ; A = 32'd45; B = 32'd234;
```

```

        @(posedge clk) c0=0 ; A = 32'd245; B = 32'd678;

        repeat(10) @(posedge clk);

    $finish;

end


always #10 clk = ~clk;

endmodule

```

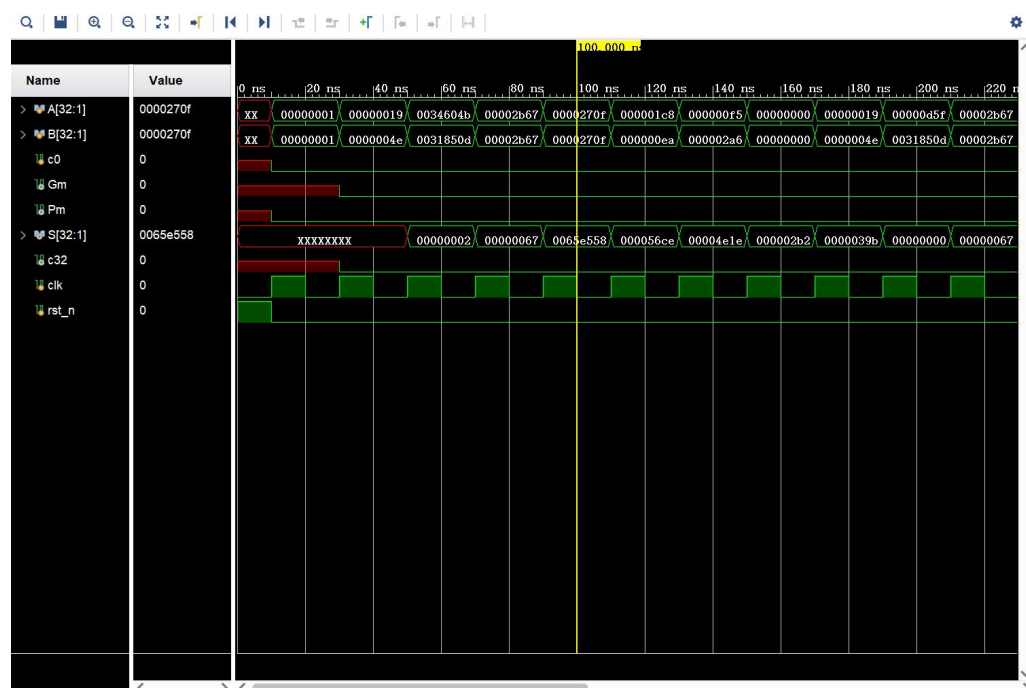
## ②仿真波形

运行行为仿真，仿真波形如下图，符合设计预期。由于该加法器的结构是二级流水线并行加法器，在一个周期内不能将两次结果计算出来再相加，所以乘法器的输出有两个周期的延迟。


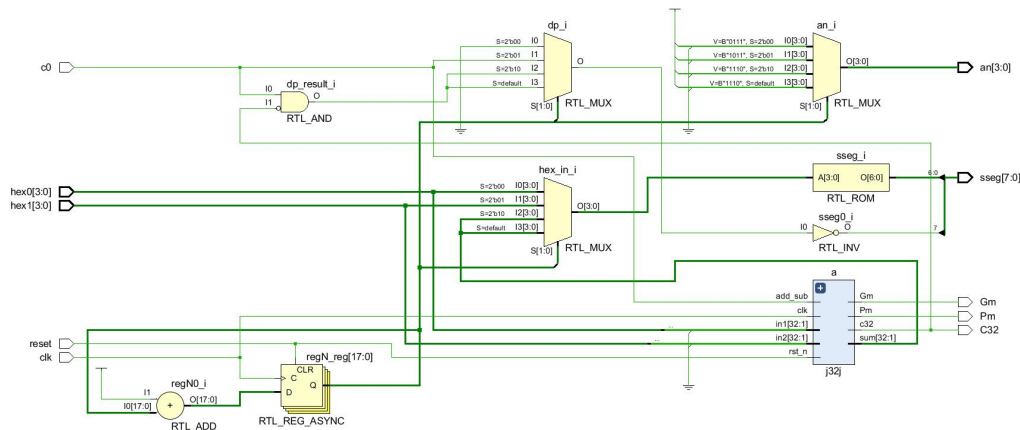
## (3) RTL 分析

利用 vivado 自带的 RTL 分析功能，对项目代码综合后进行 RTL 电路分析，如下图所示。



RTL 分析电路图

#### (4) 综合、绑定引脚、实现

约束文件如下：

```
set_property IOSTANDARD LVCMOS33 [get_ports c0]
set_property IOSTANDARD LVCMOS33 [get_ports C32]
set_property IOSTANDARD LVCMOS33 [get_ports Gm]
set_property IOSTANDARD LVCMOS33 [get_ports Pm]
set_property PACKAGE_PIN R2 [get_ports {c0}]
set_property PACKAGE_PIN P1 [get_ports {C32}]
set_property PACKAGE_PIN P3 [get_ports {Gm}]
set_property PACKAGE_PIN N3 [get_ports {Pm}]

set_property IOSTANDARD LVCMOS33 [get_ports {an[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {an[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {an[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {an[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {hex0[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {hex0[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {hex0[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {hex0[0]}]
```



```
set_property IOSTANDARD LVCMOS33 [get_ports {hex1[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {hex1[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {hex1[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {hex1[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {sseg[7]}]
set_property IOSTANDARD LVCMOS33 [get_ports {sseg[6]}]
set_property IOSTANDARD LVCMOS33 [get_ports {sseg[5]}]
set_property IOSTANDARD LVCMOS33 [get_ports {sseg[4]}]
set_property IOSTANDARD LVCMOS33 [get_ports {sseg[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {sseg[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {sseg[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {sseg[0]}]

set_property PACKAGE_PIN W4 [get_ports {an[3]}]
set_property PACKAGE_PIN V4 [get_ports {an[2]}]
set_property PACKAGE_PIN U4 [get_ports {an[1]}]
set_property PACKAGE_PIN U2 [get_ports {an[0]}]
set_property PACKAGE_PIN V17 [get_ports {hex0[0]}]
set_property PACKAGE_PIN V16 [get_ports {hex0[1]}]
set_property PACKAGE_PIN W16 [get_ports {hex0[2]}]
set_property PACKAGE_PIN W17 [get_ports {hex0[3]}]
set_property PACKAGE_PIN W15 [get_ports {hex1[0]}]
set_property PACKAGE_PIN V15 [get_ports {hex1[1]}]
set_property PACKAGE_PIN W14 [get_ports {hex1[2]}]
set_property PACKAGE_PIN W13 [get_ports {hex1[3]}]
set_property PACKAGE_PIN W7 [get_ports {sseg[6]}]
set_property PACKAGE_PIN W6 [get_ports {sseg[5]}]
set_property PACKAGE_PIN U8 [get_ports {sseg[4]}]
set_property PACKAGE_PIN V8 [get_ports {sseg[3]}]
set_property PACKAGE_PIN U5 [get_ports {sseg[2]}]
set_property PACKAGE_PIN V5 [get_ports {sseg[1]}]
set_property PACKAGE_PIN U7 [get_ports {sseg[0]}]

set_property PACKAGE_PIN V7 [get_ports {sseg[7]}]
set_property IOSTANDARD LVCMOS33 [get_ports clk]
```


```
set_property IOSTANDARD LVCMOS33 [get_ports reset]
```

```
set_property PACKAGE_PIN W5 [get_ports clk]
```

```
set_property PACKAGE_PIN U1 [get_ports reset]
```

```
set_property CLOCK_DEDICATED_ROUTE FALSE [get_nets clk]
```

(5) 生成比特流，打开硬件程序并打开硬件目标，在开发板上验证自己的逻辑程序。

 



通过实验测试，当  $\text{hex0}=2'b0001, \text{hex1}=2'b0011$  时，结果计算为 4，显示的灯结果显示正确，证明所做实验正确。

## 五、实验过程中遇到的问题及解决情况(主要问题及解决情况)

在刚开始的时候我们编写 32 位加法器的时候，没有想到使用多级加法器叠加出 32 级加法器，而是想要直接用 for 语句设计出加法器，这倒是我们代码的冗长并且极易容易出错。之后我们在绑定引脚的时候三个灯绑定重复了，导致后期上版验证的时候结果出错，后来我们调整了引脚的绑定。

## 六、实验结果及分析和（或）源程序调试过程


### 1. 本次实验的电路和功耗分析

 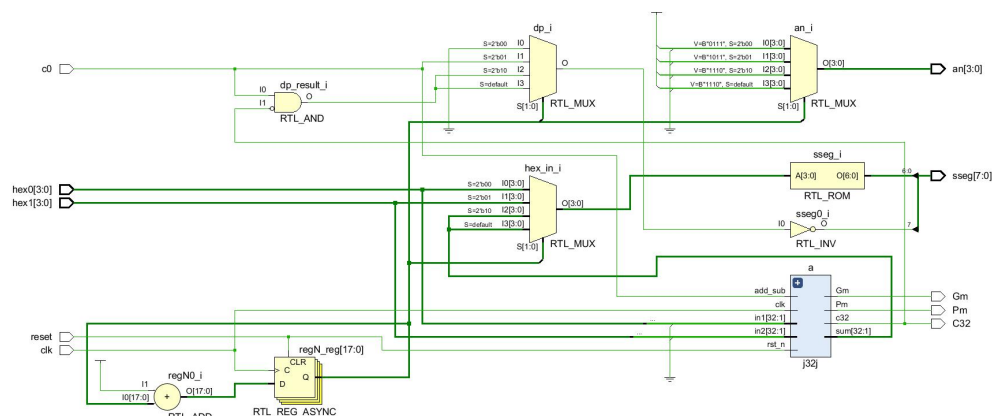

由于本次实验是 32 位的加减法器，输入输出端口较多，I/O 资源占比较大。同时本次实验中采用了流水线的结构，所以 logic 资源和 signal 资源消耗比一般的项目少。


### 2. 与实验六：加减法器的设计中的 32 位加减法器对比

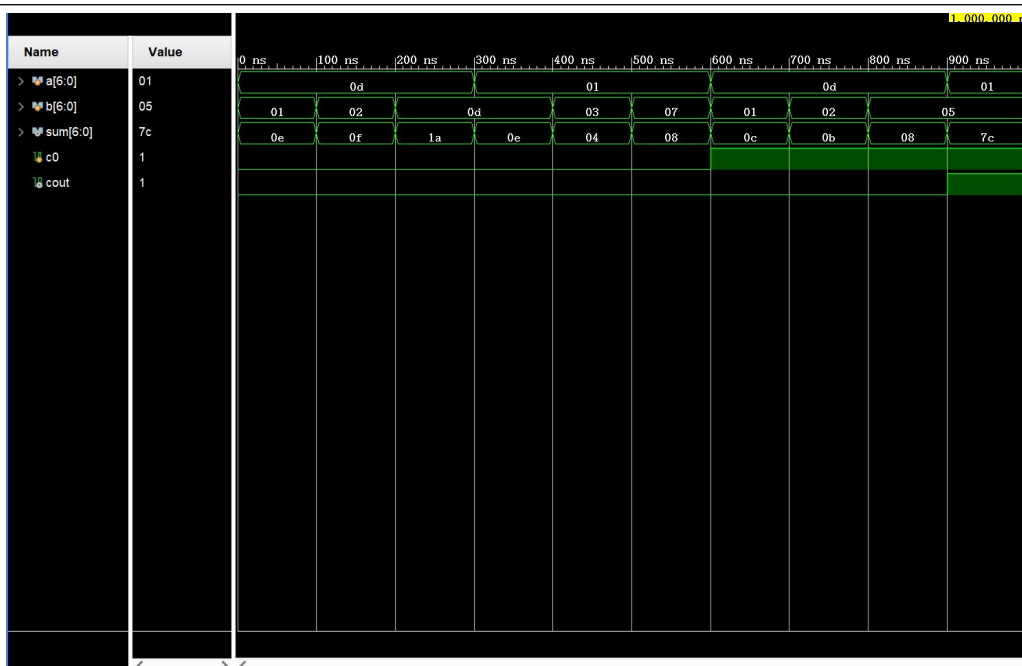(1) 从逻辑结构上，实验六中的加减法器是串行的，只有上一个加法的结果出来之后才能进行下一项的加法；而此次实验中的加减法器的流水线结构是并行的，可以同时计算加减法结果然后进行计算，效率更高，功耗更小。



### (3) 电路分析对比


实验六中的加减法器 RTL 电路分析结果如下

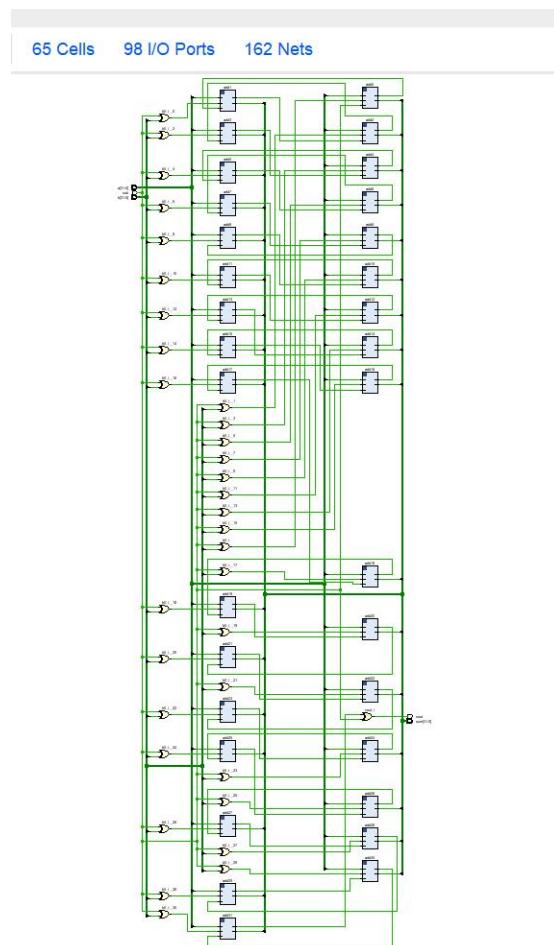

由于该电路直接由 32 个加法器串行组成，所以生成的电路相对复杂

#### (4) 功耗分析对比

实验六中的加减法器 RTL 电路分析结果如下

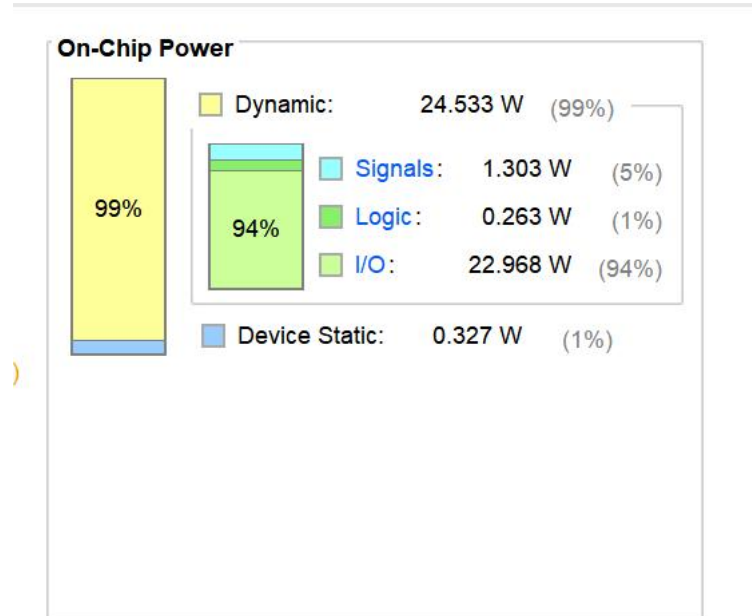

可以看到，流水加法器的两级流水线结构使得 signals 资源消耗显著减少。

#### 七、小组分工情况说明

：编写 32 位流水线加法器设计的顶层代码，并进行仿真验证。共同分析在 RTL 分析、逻辑 资源占用、功耗上的问题。

：编写 32 位流水线加法器的 4 位加法器和 CLA 代码，并进行仿真验证。共同分析在 RTL 分析、逻辑 资源占用、功耗上的问题。

：编写实验六的组合逻辑加减法器代码，编写系统加法器的代码，完成引脚 绑定和上板验证。共同分析在 RTL 分析、逻辑 资源占用、功耗上的问题。

